



Cairo University
Faculty of Computers and Artificial Intelligence



CS322

Computer Architecture and Organization

Assignment 2

Instructor: Dr. Mohammad El-Ramly

Team members:

Abdelrahman Nasr Abdelsalam Ali 20170343

Bahaa El Deen Osama Sayed 20170078

Task 2

Problem 3.31 = 4.42 (Bahaa El-Deen Osama):

State Transition Table

| Current State | Input | Next State |
|---------------|-------|------------|
| S00 | 0 | S01 |
| S00 | 1 | S11 |
| S01 | 0 | S00 |
| S01 | 1 | S10 |
| S10 | 0 | S10 |
| S10 | 1 | S01 |
| S11 | 0 | S11 |
| S11 | 1 | S01 |

Output Table



| State | Output |
|-------|--------|
| S00 | 0 |
| S01 | 1 |
| S1X | 1 |

```

module FSM4_42(input logic clk, input logic reset, input logic x, output logic y);
    typedef enum logic [1:0] {S00, S01, S10, S11} statetype;
    statetype [1:0] state, nextstate;
    //State register
    always_ff@(posedge clk ,posedge reset)
        if(reset) state <= S00;
        else      state <= nextstate;
    // next state logic
    always_comb
        case(state)
            S00: if(x) nextstate = S11;
                else nextstate=S01;
            S01: if(x) nextstate=S10;
                else nextstate=S00;
            S10: if(x) nextstate=S01;
                else nextstate=S10;
            S11: if(x) nextstate=S01;
                else nextstate=S11;
            default: nextstate=S00;
        endcase
    //output logic
    assign y = (state==S11 ) | (state==S01) | (state==S10);
endmodule

```

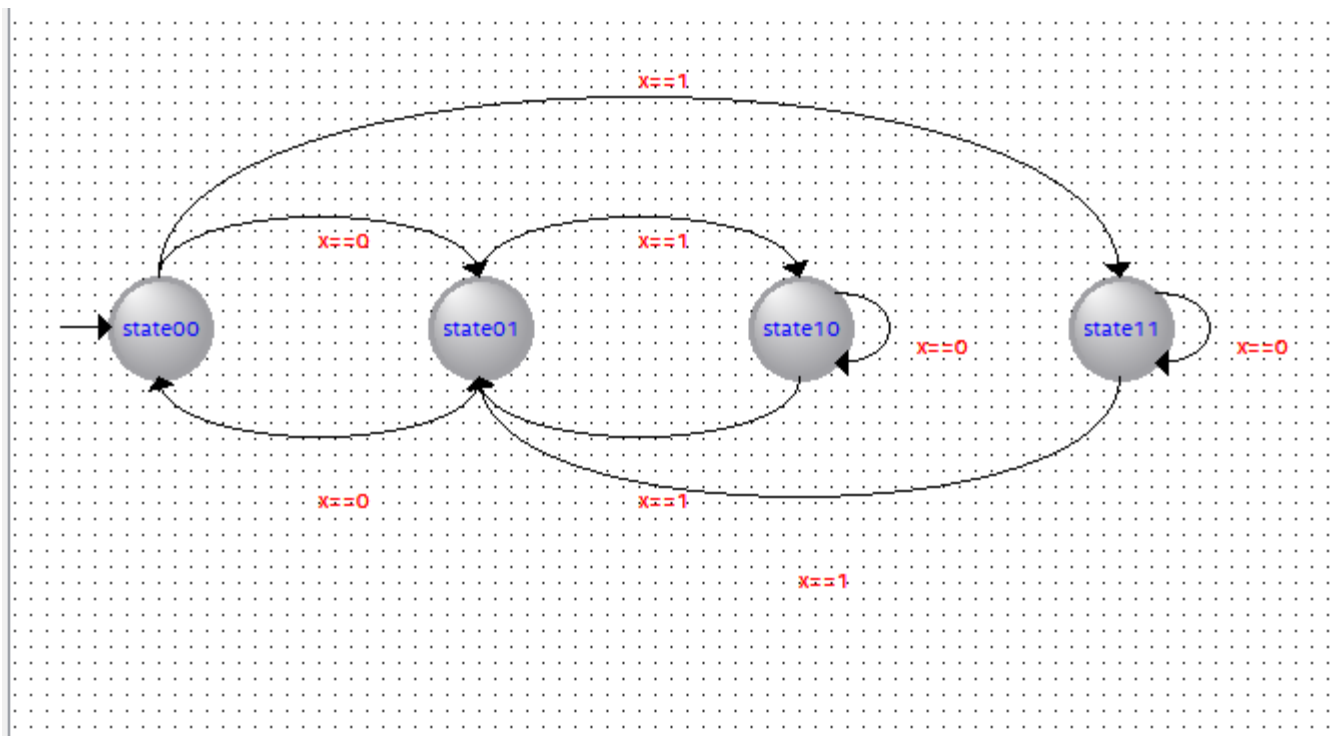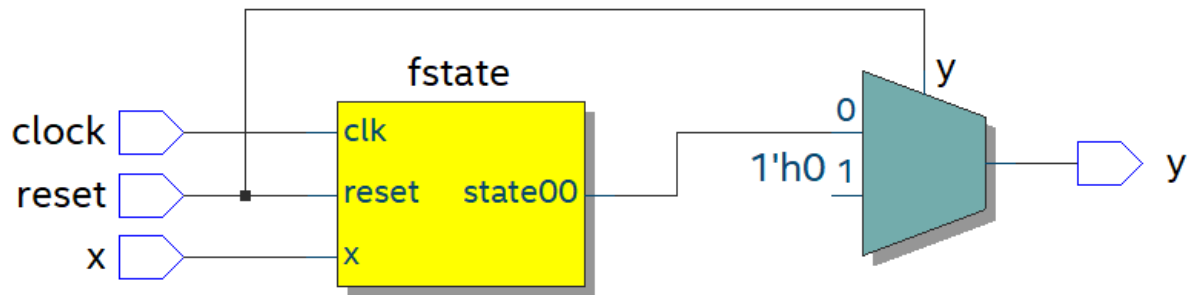The schematic diagram (resulting from synthesizing the code on Quartus):



Note: The output is TRUE only and only if the nextstate S01 or S1X (X is don't care)

Problem 3.32 (Abdelrahman Nasr):


State Transition Table

| Current State | Input | Next State |
|---------------|-------|------------|
| S0 | 0 | S0 |
| S0 | 1 | S1 |
| S1 | 0 | S0 |
| S1 | 1 | S2 |
| S2 | 0 | S0 |
| S2 | 1 | S2 |

Output Table

| State | Input |
|-------|-------|
| S0 | 0 |
| S1 | 0 |
| S2 | 1 |

State Transition Diagram

 

```

module FSM32Ex(input logic clk, input logic reset, input logic x, output logic y);

    typedef enum logic [1:0] {S0, S1, S2} statetype;
    statetype state, nextstate;

    // state register
    always_ff @(posedge clk, posedge reset)
        if (reset) state <= S0;
        else state <= nextstate;


    // next state logic
    always_comb
        case (state)
            S0:    if (x) nextstate = S1;
                   else    nextstate = S0;
            S1:    if (x) nextstate = S2;
                   else    nextstate = S0;
            S2:    if (x) nextstate = S2;
                   else    nextstate = S0;
            default: nextstate <= S0;
        endcase

    // output logic
    assign y = (state == S2);
endmodule


```

Description: The FSM output is TRUE whenever the input is TRUE followed by another TRUE input and FALSE otherwise.

 The schematic diagram (resulting from synthesizing the code on Quartus):



The simulation results on ModelSim:

 


Problem 4.44 (Abdelrahman Nasr):

```
module register(input logic in, input logic clock, output logic out);  
always_ff @(posedge clock)  
    out <= in;  
endmodule
```

```
module EX44(input logic [3:0] a, input logic clk, output logic out);  
    logic [3:0] b;  
    logic y;  
    // inputs to registers  
    register r1(a[3], clk, b[3]);  
    register r2(a[2], clk, b[2]);  
    register r3(a[1], clk, b[1]);  
    register r4(a[0], clk, b[0]);  
    // XORing  
    assign y = ((b[3] ^ b[2]) ^ b[1]) ^ b[0];  
    // storing output  
    register rout(y, clk, out);  
endmodule
```

Description: The four inputs are passed first to registers to store their values, then all of them are XORed using 3 XOR gates and storing the output in a register too.

 The schematic diagram (resulting from synthesizing the code on Quartus):



The simulation results on ModelSim:




Note: The output is TRUE only and only if there are odd number of TRUE inputs and false otherwise

Problem 4.46 (Bahaa EL-Deen Osama):


There can be several drivers for a signal declared as tri.

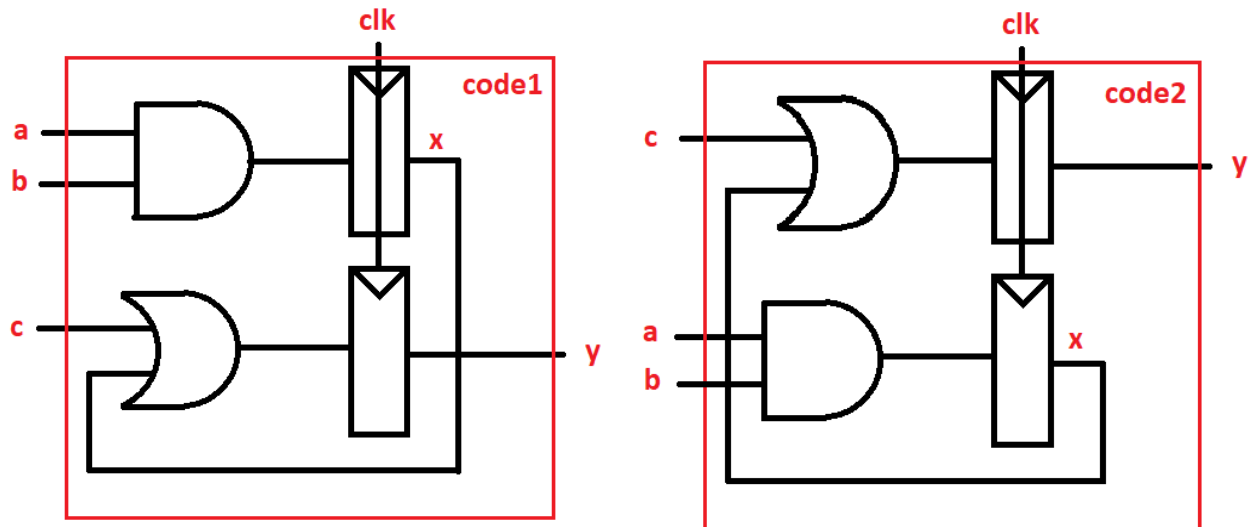Problem 4.48 (Abdelrahman Nasr):

Yes, they both have the same functionality



Testbench simulation for different values:

 

Problem 4.50 (Bahaa El-Deen Osama):

(a)

```
module latch(input logic clk ,input logic [3:0] d, output reg [3:0] q);  
    always @(clk)  
        if (clk) q <= d;  
endmodule
```

Errors:

1. Output reg[3:0]q must be output logic reg[3:0].
2. Always @(clk) must be always_latch.

Fixed Code:

```
module latch(input logic clk ,input logic [3:0] d, output logic reg [3:0] q);  
    always_latch  
        if (clk) q <= d;  
endmodule
```

(b)

```
module gates(input logic [3:0] a, b, output logic [3:0] y1, y2, y3, y4, y5);  
    always @(a)  
    begin  
        y1 = a & b;  
        y2 = a | b;  
        y3 = a ^ b;  
        y4 = ~(a & b);  
        y5 = ~(a | b);  
    end  
endmodule
```

Error: always @(a) must be always_comb .

Fixed Code:

```
module gates(input logic [3:0] a, b, output logic [3:0] y1, y2, y3, y4, y5);  
    always_comb  
    begin
```

```

    y1 = a & b;
    y2 = a | b;
    y3 = a ^ b;
    y4 = ~(a & b);
    y5 = ~(a | b);
end
endmodule

```

(c)

```

module mux2(input logic [3:0] d0, d1, input logic s, output logic [3:0] y);
    always @(posedge s)
        if (s) y <= d1;
        else y <= d0;
endmodule

```

Error: always @(posedge s) must be always_comb

Fixed Code:

```

module mux2(input logic [3:0] d0, d1, input logic s, output logic [3:0] y);
    always_comb
        if (s) y = d1;
        else y = d0;
endmodule

```

(d)

```

module twoflops(input logic clk, input logic d0, d1, output logic q0, q1);
    always @(posedge clk)
        q1 = d1;
        q0 = d0;
endmodule

```

Error: always@(posedge clk) must be always_ff@(posedge clk)

Fixed Code:

```

module twoflops(input logic clk , input logic d0, d1, output logic q0, q1);
    always_ff @(posedge clk)
        begin
            q1 <= d1;
            q0 <= d0;
        end
endmodule

```

```
        end
    endmodule
```

(e)

```
module FSM(input logic clk, input logic a, output logic out1, out2);
    logic state;
    // next state logic and register (sequential)
    always_ff @(posedge clk)
        if (state == 0) begin
            if (a) state <= 1;
        end else begin
            if (~a) state <= 0;
        end
    always_comb
    // output logic (combinational)
    if (state == 0) out1 = 1;
    else out2 = 1;
endmodule
```

Error: module messing state logic and input declaration.

Fixed Code:

```
module FSM(input logic clk, input logic reset ,input logic a, output logic out1, out2);
    logic state ,nextstate;

    // state register
    always_ff @(posedge clk , posedge reset)
        if (reset) state <= 1'b0;           //first state
        else state <= nextstate;           //second state

    // next state logic
    always_comb
    case(state)
        1'b0 :      if (a) nextstate =1'b1;
                    else nextstate = 1'b0;
        1'b1:      if(a) nextstate =1'b1;
                    else nextstate =1'b0;

    // output logic (combinational)
    Always_comb
    if (state == 0) {out1,out2} = {1b'1 , 1'b0};
    else {out1,out2} = { 1b'0 ,1'b1};
endmodule
```

Problem 4.50 (Abdelrahman Nasr):

(f)

```
module priority(input logic [3:0] a, output logic [3:0] y);
    always_comb
        if (a[3]) y = 4'b1000;
        else if (a[2]) y = 4'b0100;
        else if (a[1]) y = 4'b0010;
        else if (a[0]) y = 4'b0001;
endmodule
```

Errors:

3. priority is a reserved keyword on SystemVerilog
4. There must be a default statement for the if condition to prevent conflicts

Fixed Code:

```
module priority_check(input logic [3:0] a, output logic [3:0] y);
    always_comb
        if (a[3]) y = 4'b1000;
        else if (a[2]) y = 4'b0100;
        else if (a[1]) y = 4'b0010;
        else if (a[0]) y = 4'b0001;
        else y = 4'b0000;
endmodule
```

(g)

```
module divideby3FSM(input logic clk, input logic reset, output logic out);
    logic [1:0] state, nextstate;
    parameter S0 = 2'b00;
    parameter S1 = 2'b01;
    parameter S2 = 2'b10;
    // State Register
    always_ff @(posedge clk, posedge reset)
        if (reset) state <= S0;
        else state <= nextstate;
    // Next State Logic
    always @(state)
        case (state)
            S0: nextstate = S1;
            S1: nextstate = S2;
            S2: nextstate = S0;
        endcase
    // Output Logic
```

```

        assign out = (state == S2);
    endmodule

```

Errors:

1. always @(state) should be always_comb to avoid missing signals in the sensitivity list
2. the case statement is missing the default case

Fixed Code:

```

module divideby3FSM(input logic clk, input logic reset, output logic out);
    logic [1:0] state, nextstate;
    parameter S0 = 2'b00;
    parameter S1 = 2'b01;
    parameter S2 = 2'b10;
    // State Register
    always_ff @(posedge clk, posedge reset)
        if (reset) state <= S0;
        else state <= nextstate;
    // Next State Logic
    always_comb
        case (state)
            S0: nextstate = S1;
            S1: nextstate = S2;
            S2: nextstate = S0;
            default nextstate = S0;
        endcase
    // Output Logic
    assign out = (state == S2);
endmodule

```

(h)

```

module mux2tri(input logic [3:0] d0, d1, input logic s, output tri [3:0] y);
    tristate t0(d0, s, y);
    tristate t1(d1, s, y);
endmodule

```

Error: It's a logical error because s parameter of t0 instance should be passed inverted

Fixed Code:

```

module mux2tri(input logic [3:0] d0, d1, input logic s, output tri [3:0] y);
    tristate t0(d0, ~s, y);
    tristate t1(d1, s, y);
endmodule

```

(i)

```
module floprsen(input logic clk, input logic reset, input logic set, input logic [3:0] d, output logic [3:0] q);
    always_ff @(posedge clk, posedge reset)
        if (reset) q <= 0;
        else q <= d;
    always @(set)
        if (set) q <= 1;
endmodule
```

Error: The output is assigned multiple times which cause conflicts to the output's signal

Fixed Code:

```
module floprsen(input logic clk, input logic reset, input logic set, input logic [3:0] d, output logic [3:0] q);
    always_ff @(posedge clk, posedge reset, posedge set)
        if (reset) q <= 0;
        else if (set) q<=1;
        else q <= d;
endmodule
```

(j)

```
module and3(input logic a, b, c, output logic y);
    logic tmp;
    always @(a, b, c)
    begin
        tmp <= a & b;
        y <= tmp & c;
    end
endmodule
```

Errors:

1. always_comb should be used instead of always @(a, b, c) to avoid missing signals in the sensitivity list
2. The blocking assignment should be used with always_comb


Fixed Code:

```
module and3(input logic a, b, c, output logic y);
    logic tmp;
    always_comb
    begin
        tmp = a & b;
        y = tmp & c;
    end
endmodule
```


Task 3 – FP Multiplier

```
module FP_mul(input logic [31:0] x, y, output logic [31:0] m);  
    // internal variables  
    logic [23:0] mantx, manty;  
    logic [7:0] exponent, expx, expy;  
    logic [22:0] fraction;  
    logic [47:0] result;  
  
    // extracting to exponent and mantisa  
    assign expx = x[30:23];  
    assign mantx = {1'b1, x[22:0]};  
    assign expy = y[30:23];  
    assign manty = {1'b1, y[22:0]};  
  
    // multiplying mantisas and calculating the new fraction and exponent  
    assign result = mantx * manty;  
    assign fraction = result[47] ? result[46:24] : result[45:23];  
    assign exponent = result[47] ? (expx + expy - 126) : (expx + expy - 127);  
  
    // the result of multiplication  
    assign m = {1'b0, exponent, fraction};  
  
endmodule
```

Simulation:

 

Task 4 - ALU

Problem 5.9:

```
module ALU5_9(input logic [31:0]a, input logic [31:0]b, input logic [2:0]f, output logic [31:0]y);
```

```
// ALU operations:
// -----
// 000 = A AND B
// 001 = A OR B
// 010 = A + B
// 011 = Not Used
// 100 = A AND B'
// 101 = A OR B'
// 110 = A - B
// 111 = SLT
```


```
logic[31:0] sum, B_output;
```


```
assign B_output = (f[2]) ? ~b : b;
assign sum = a+B_output+f[2];
```

```
always_comb
    case(f[1:0])
        2'b00: y <= a & B_output; // AND operation
        2'b01: y <= a | B_output; // OR operation
        2'b10: y <= sum; // Sumation
        2'b11: y <= sum[31];
        default: y<= sum[31];
    endcase
```

```
endmodule
```

Simulation:

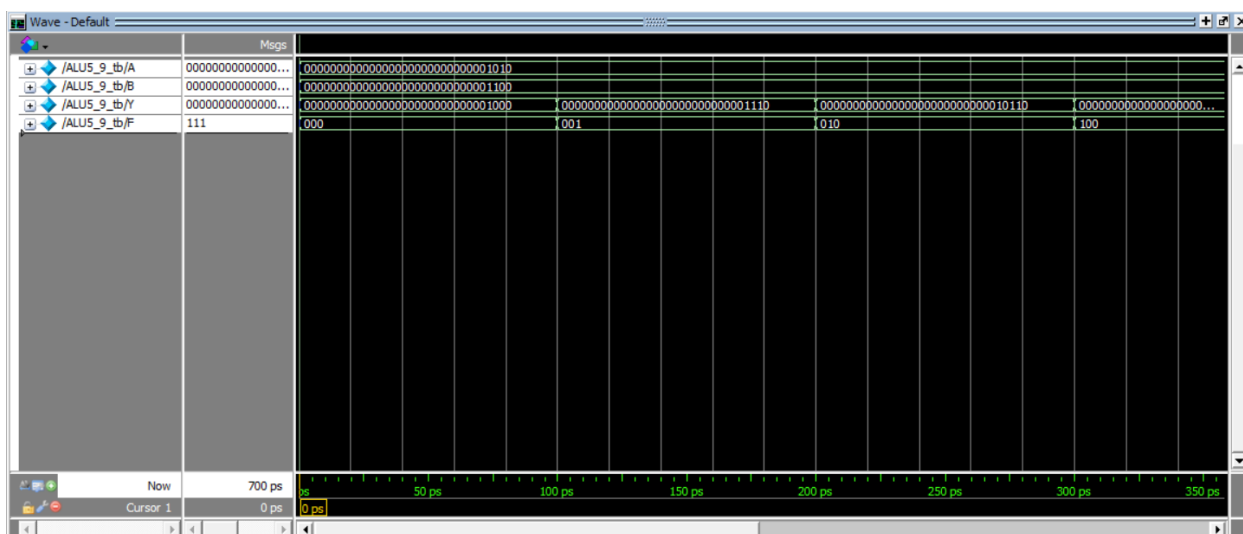

 


Problem 5.10:

(a) The overflow equation:

$$\sim f[2] \& (a \& b \& \sim s[31] \mid \sim a \& \sim b \& s[31]) \mid f[2] \& (\sim a \& b \& s[31] \mid a \& \sim b \& \sim s[31]);$$

(b) Circuit Diagram:

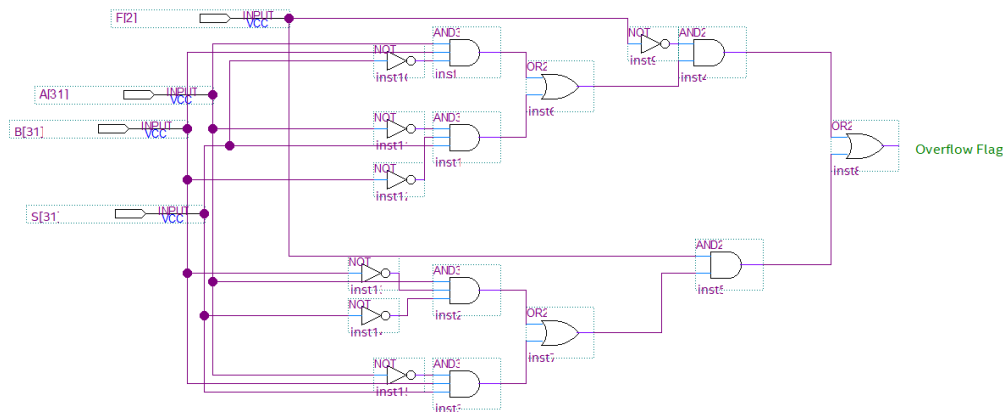

```
module ALU5_10(input logic [31:0]a, input logic [31:0]b, input logic [2:0]f, output logic [31:0]y, output logic overflow);
```

```
// ALU operations:
// -----
// 000 = A AND B
// 001 = A OR B
// 010 = A + B
// 011 = Not Used
// 100 = A AND B'
// 101 = A OR B'
// 110 = A - B
// 111 = SLT
```

```
logic[31:0] sum, B_output;
```

```

assign B_output = (f[2]) ? ~b : b;
assign sum = a+B_output+f[2];


always_comb
    case(f[1:0])
        2'b00: y <= a & B_output;      // AND operation
        2'b01: y <= a | B_output;      // OR operation
        2'b10: y <= sum;               // Sumation
        2'b11: y <= sum[31];
        default: y<= sum[31];
    endcase

always_comb
    case (f[2])
        1'b0: overflow = a[31] & b[31] & ~sum[31] | ~a[31] & ~b[31] & sum[31];
        1'b1: overflow = ~a[31] & b[31] & sum[31] | a[31] & ~b[31] & ~sum[31];
        default: overflow = 0;
    endcase

endmodule

```

Simulation:

 

Problem 5.11:

```

module ALU5_11(input logic [31:0]a, input logic [31:0]b, input logic [2:0]f, output logic
[31:0]y, output logic zero);

    // ALU operations:
    // -----
    // 000 = A AND B
    // 001 = A OR B
    // 010 = A + B

```

```

// 011 = Not Used
// 100 = A AND B'
// 101 = A OR B'
// 110 = A - B
// 111 = SLT

    logic[31:0] sum, B_output;

    assign B_output = (f[2]) ? ~b : b;
    assign sum = a+B_output+f[2];


    always_comb
        case(f[1:0])
            2'b00: y <= a & B_output;      // AND operation
            2'b01: y <= a | B_output;      // OR operation
            2'b10: y <= sum;                // Sumation
            2'b11: y <= sum[31];
            default: y<= sum[31];
        endcase

    assign zero = (y==32'b0);

endmodule

```

Simulation:

 

Problem 5.12 (Testbenches):

```

module ALU5_9_tb();

    logic[31:0] A, B, Y;
    logic[2:0] F;

    // instantiate device under test

```

```
ALU5_9 dut(A, B, F, Y);

initial begin
    A<=32'b0000000000000000000000000000001010;
    B<=32'b0000000000000000000000000000001100;

    F<=3'b000; #100;
    F<=3'b001; #100;
    F<=3'b010; #100;

    F<=3'b100; #100;
    F<=3'b101; #100;
    F<=3'b110; #100;
    F<=3'b111; #100;
end

endmodule


module ALU5_10_tb();

    logic[31:0] A, B, Y;
    logic[2:0] F;

    // Flags
    logic VF;

    // instantiate device under test
    ALU5_11 dut(A, B, F, Y, VF);

    initial begin
        A<=32'b01111111111111111111111111111111;
        B<=32'b00000000000000000000000000000001;
        F<=3'b010; #100;

        A<=32'b011111111111111111111111111111110;
        F<=3'b010; #100;
    end

endmodule


module ALU5_11_tb();

    logic[31:0] A, B, Y;
    logic[2:0] F;

    // Flags
    logic ZF;

    // instantiate device under test
    ALU5_11 dut(A, B, F, Y, ZF);

    initial begin
        A<=32'b00000000000000000000000000000001;
        B<=32'b00000000000000000000000000000001;
        F<=3'b110; #100;

        B<=32'b00000000000000000000000000000010;
        F<=3'b110; #100;
    end

endmodule
```